

# Electricity

Name: \_\_\_\_\_

## Vocabulary Words

Match the definition to the correct vocabulary word.

- |  |                |
|--|----------------|
| 1. ___ Made up of electrons and flows, like water, through wires     | A. Conductor   |
| 2. ___ A material that does not allow electricity to pass through it | B. Insulator   |
| 3. ___ The amount of electrons flowing in a circuit                  | C. Current     |
| 4. ___ A material that allows electricity to pass through it         | D. Electricity |

## Closed or Open Circuit?

Determine which circuits are open or closed. Will the bulb light?

